



# EE479L Fall 2018 Design Project#1 Report

## CMOS Amplifier Design with 30dB DC Gain

HONGXIANG GAO 8095639536

MINGYANG LI 3349336154

*University of Southern California*

October 6, 2018

### Introduction

Amplifiers abound in the devices we use in our day to day life, such as stereos, loud speakers and cellphones[1]. The purpose of an amplifier is to increase the power in a signal without distorting it. This process is called amplification. For example, amplifiers are used to increase the power in the signal from a microphone so that it can drive a loud speaker[2]. There are many kinds of amplifiers we are now using in circuits design, such as wideband amplifiers, RF amplifiers and so on. These kinds of amplifiers hold different functions because of their distinct configurations and parameter settings.

In this case, our purpose is to amplify a small signal with an magnification of 30 in decibel.

### Design Concept

#### Stage Design

In this project, we are going to design the amplifier with DC gain as 30dB, which is about 31.62 in standard unit. We will need to reach this target by applying common source, common drain and common gate configurations. For these three fundamental amplifiers, the common source configuration is the best suited for realizing the bulk of the gain required design; the common gate configuration has a low input resistance, which makes it only useful in some specific applications such as RF circuits; the common drain (source follower) configuration works as a voltage buffer for connecting a high-resistance source to a low-resistance load, its purpose is to equip the



amplifier with a low output resistance[3].

In this project, we will apply the common source configuration to meet the high gain requirement and the common drain configuration as a buffer stage since the output impedance of the common source stage is too high while the load resistance is very low. For each stage, there will be a capacitor to isolate the DC voltage. Figure (1) shows the basic structure of the circuit.

 


Figure 1: Stage Design of the Circuit

### Parameters Extraction of the Transistor

To design the stages of the circuit, firstly we will need to find out the parameters of the transistor such as  $\mu_n$ ,  $C_{ox}$  and  $V_{th}$ . To get these parameters, we test the performance of the transistor under different conditions and extract these parameters by applying the current expression as in Eq (1).

$$I_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \quad (1)$$

The test circuit is shown in Figure (2).

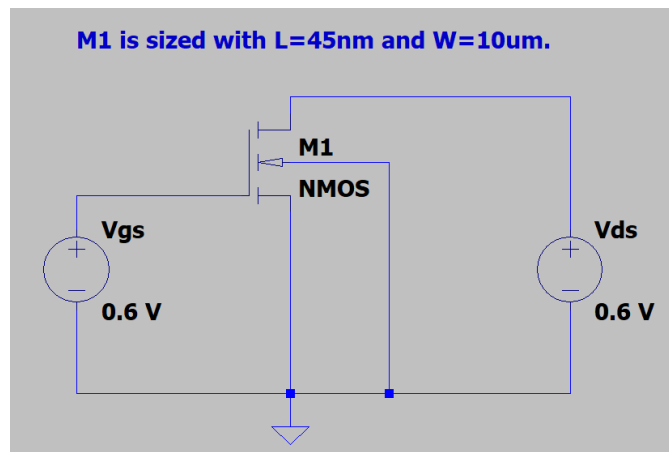


Figure 2: Test Circuit



Then we have the characteristic curves of the transistor. Figure (3) shows the  $I_d - V_{gs}$  relation under different  $V_{DS}$  conditions ranges from 0.1V to 0.8V. And we can find that the threshold voltage of the transistor is about  $V_{th} \approx 0.42V$ .

 


Figure 3:  $I_d - V_{gs}$  Relation with Variant  $V_{DS}$

Figure (4) shows the  $I_d - V_{DS}$  relation with  $V_{gs}$  ranges from 0.1V to 0.8V. The channel length modulation constant is about  $\lambda \approx 0.055V^{-1}$  by Eq (2). From Eq (1), the value of the carrier constant is about  $k' = \mu_n C_{ox} \approx 0.483mA/V^2$ .

$$\frac{1}{r_o} = \frac{\partial I_d}{\partial V_{DS}} = \lambda I_d \quad (2)$$

 


Figure 4:  $I_d - V_{DS}$  Relation with variant  $V_{gs}$

In this figure, the channel length modulation resistance is only about  $r_o \approx 3600\Omega$ , which is small value. To get a high gain of a common source configuration,  $r_o = 3600\Omega$  is not enough, a method to enlarge this value is needed. Since the value of  $r_o$  is given by Eq (2). To increase the value of  $r_o$ , one way is to decrease the value of  $I_d$ , the other one is to decrease  $\lambda$ . Both of



them depend on the structure of the transistor, say the value of the channel length  $L$  and width  $W$ .

 


Figure 5:  $I_d - V_{DS}$  Relation with Variant  $W$ ,  $L=100\text{nm}$

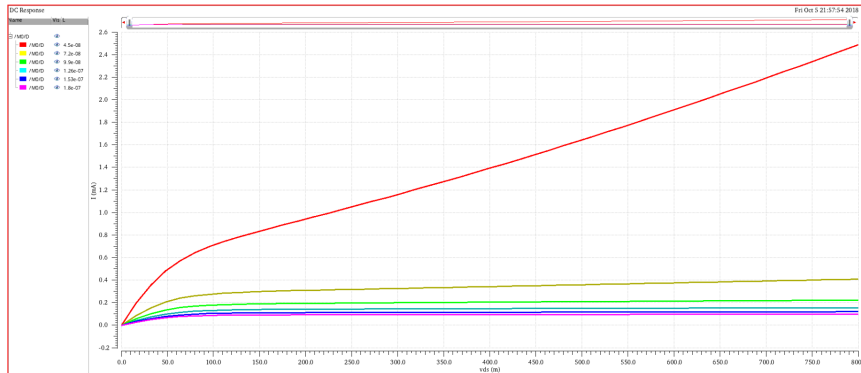


Figure 6:  $I_d - V_{DS}$  Relation with Variant  $L$ ,  $W=10\mu\text{m}$

After trying different channel length and width, Figure (5) shows the  $I_d - V_{DS}$  curve with different channel width  $W$  ranges from  $10\mu\text{m}$  to  $60\mu\text{m}$  with the channel length as  $100\text{nm}$ , and Figure (6) shows the  $I_d - V_{DS}$  curve with different channel length  $L$  ranges from  $45\text{nm}$  to  $180\text{nm}$  with the channel width as  $10\mu\text{m}$ . In both cases, the value of  $V_{gs}$  and  $V_{ds}$  are set as  $0.5\text{V}$ . The value of  $r_o$  is shown in Table (1) and Table (2). The value of  $r_o$  is proportional to  $\frac{1}{W}$  since the value of  $r_o = \frac{2}{\lambda \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2}$ . However, the value of  $r_o$  increase greatly as the value of  $L$  increases not only because  $L$  term is proportional to  $r_o$ , but also it will effect the CLM constant  $\lambda$ . To ensure that the value of  $r_o$  will not effect the amplification in the common source stage, the value of  $r_o$  should be greater than  $100\text{k}\Omega$ , since in most cases the value of  $R_D$  is about several  $\text{k}\Omega$ s, we decide to use the transistor with  $L=180\text{nm}$  which will lead to a greater  $r_o$ .

Table 1:  $r_o$  with Different  $W$ 

$W$ ( $\mu\mathbf{m}$ )	$r_o$ ( $\Omega$ )
10	22.53k
20	11.42k
30	7.61k
40	5.63k
50	4.55k
60	3.78k

Table 2:  $r_o$  with Different  $L$ 

$L$ ( $\mathbf{nm}$ )	$r_o$ ( $\Omega$ )
45	0.42k
72	6.02k
99	22.18k
126	46.15k
153	76.59k
180	118.48k

For transistors with channel length  $L=180\text{nm}$ , its performance parameters are shown in Table (3).

Table 3: Parameter Extration of  $L=180\text{nm}$ ,  $W=30\mu\text{m}$  Transistor

$V_{th}$ ( $\mathbf{V}$ )	$\mu_n C_{ox}$ ( $\mathbf{mA/V^2}$ )	$\lambda$ ( $\mathbf{V^{-1}}$ )
0.392	0.285	0.086

## Common Source Configuration Design

 


Figure 7: Common Source Configuration

The common source configuration is shown in Figure 7. The amplification coefficient is defined as Eq (3), where  $g_m$  is expressed in Eq (4).

$$\|A_v\| = G_m R_{out} = g_m (r_o // R_D) \approx g_m R_D \quad (3)$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})(1 + \lambda V_{DS}) = \frac{2I_D}{V_{GS} - V_{th}} \quad (4)$$

According to Kirchhoff Voltage Law,

$$V_{DS} = V_{DD} - I_d R_D \quad (5)$$



Substitute Eq (4) and Eq(5) to Eq (3),

$$\|A_v\| = \frac{2I_D}{V_{GS} - V_{th}} \times \frac{V_{DD} - V_{DS}}{I_D} = \frac{2(V_{DD} - V_{DS})}{V_{GS} - V_{th}} \quad (6)$$

To increase the gain,  $V_{DS}$  should be decreased as much as possible and  $V_{GS}$  should be close to the threshold voltage  $V_{th}$ . In this case, the value we choose is as in Table (4).

Table 4: Parameter Setting in Common Source Configuration

$V_{GS}$ (mV)	$W$ ( $\mu\text{m}$ )	$V_{DS}$ (mV)
490	30	200

Then according to Eq (1) and Eq (3),

$$\begin{aligned} I_d &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \\ &= \frac{1}{2} \times 0.285^{-3} \times \frac{30 \times 10^{-6}}{180 \times 10^{-9}} (0.49 - 0.392)^2 (1 + 0.086 \times 0.2) \\ &= 232 \times 10^{-6} \text{ A} \end{aligned}$$

$$R_d = \frac{V_{DD} - V_{DS}}{I_d} = \frac{0.8 - 0.2}{232 \times 10^{-6}} = 2.57 \text{ k}\Omega$$

$$\|A_v\| = \frac{2(V_{DD} - V_{DS})}{V_{GS} - V_{th}} = \frac{2(0.8 - 0.2)}{0.49 - 0.392} \approx 12.24 = 21.76 \text{ dB}$$

Large signal simulation after setting the value of  $V_{GS}$ ,  $W$  and  $R_D$  is shown in Large Circuit Section with Figure (13). Figure (8) is the AC voltage gain simulation result.



Figure 8: AC Gain Simulation Result of CS Stage

Table 5: Hand-Calculation vs Simulation Result in CS Stage

	$V_{GS}$ (mV)	$V_{DS}$ (mV)	$I_d$ (A)	$A_v$ (dB)
Hand-Calculation	490	200	$232 \times 10^{-6}$	21.76
Simulation	488	203	$232.2 \times 10^{-6}$	18.73

Table (5) shows the hand-calculation result and the simulation result.

For large signal analysis, the result in hand-calculation is almost the same with the simulation result while for the AC gain, they are different slightly, which is about 3dB.

There are many reasons that could lead to this result.

1. The existence of  $r_o$ . The value of  $r_o$  in this case is about  $38k\Omega$ , which will lead to a decrease about 0.57dB.
2. The carrier mobility  $\mu_n$  may fluctuate slightly due to the different current flow.

Since the AC gain is about 18.5dB, so we will need two common source stages to realize the 30dB gain requirement.

### Common Drain Configuration Design

 


Figure 9: Common Drain Configuration

The common source configuration is shown in Figure 9. The amplification coefficient is defined as Eq (8), where  $g_m$  is expressed in Eq (4).

$$A_v = G_m R_{out} = \frac{g_m R_S}{1 + g_m R_S} \left( \frac{1}{g_m} // \frac{1}{g_{mb}} // r_o // R_S \right) \quad (7)$$

The output voltage on the load will be

$$A_{vload} = A_v \times \frac{R_{load}}{R_{out} + R_{load}} \quad (8)$$



To make this stage as a perfect buffer stage, the output resistance should be as small as possible and enlarge the value of  $g_m$ . The expression of  $g_m$  is given in Eq (4), which is proportional to  $\frac{W}{L}$ . Meanwhile, the value of  $r_o$  also has a great effect on the value  $R_{out}$ , and the value of  $r_o$  decreases greatly as  $\frac{W}{L}$  increases. So in this case we choose a large  $W$  as  $80\mu\text{m}$  and a small channel length as  $L = 45\text{nm}$ . And of course to enlarge  $g_m$ , the value of  $V_{GS}$  is also set as a large value. Table (6)

Table 6: Parameter Setting in Common Drain Configuration

$V_{GS}$ (mV)	$W$ ( $\mu\text{m}$ )	$L$ (nm)	$R_S$ ( $\Omega$ )
680	80	45	125

Then according to Eq (1) and Eq (4),

$$\begin{aligned} I_d &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \\ &\approx \frac{1}{2} \times 0.285^{-3} \times \frac{80 \times 10^{-6}}{45 \times 10^{-9}} (0.68 - 0.392)^2 \\ &= 2.10 \times 10^{-3} \text{A} \end{aligned}$$

$$\begin{aligned} g_m &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) (1 + \lambda V_{DS}) \\ &\approx 0.285^{-3} \times \frac{80 \times 10^{-6}}{45 \times 10^{-9}} (0.68 - 0.392) \\ &= 0.0146 \text{A/V} \end{aligned}$$

$$V_{DS} = V_{DD} - I_{DS} R_S = 0.8 - 2.1 \times 10^{-3} \times 125 = 537.5 \text{mV}$$

Then the output resistance is

$$R_{out} = \frac{1}{g_m} // \frac{1}{g_{mb}} // r_o // R_S \approx 125 // 68.5 = 44.25 \Omega$$

The short-circuit transconductance is

$$G_M = \frac{g_m R_S}{1 + g_m R_S} = \frac{0.0146 \times 125}{1 + 0.0146 \times 125} = 0.65$$

Then the common drain amplification is

$$A_{vload} = G_M \frac{R_{load}}{R_{out} + R_{load}} = 0.65 \times \frac{50}{44.25 + 50} = 0.35 = -9.11 \text{dB}$$

Large signal simulation after setting the value of  $V_{GS}$ ,  $W$  and  $R_D$  is shown in Large Circuit Section with Figure (13). Figure (10) is the AC voltage gain simulation result.



 


Figure 10: AC Gain Simulation Result of CD Stage

Table 7: Hand-Calculation vs Simulation Result in CD Stage

	$V_{GS}$ (mV)	$V_{DS}$ (mV)	$I_d$ (A)	$A_{vload}$ (dB)
Hand-Calculation	680.0	537.5	$2.100 \times 10^{-3}$	-9.11
Simulation	679.6	543.3	$2.085 \times 10^{-3}$	-6.97

Table (7) shows the hand-calculation result and the simulation result.

For large signal analysis, the result in hand-calculation is almost the same with the simulation result while for the AC gain, they are different slightly, which is about 2.14dB. The simulation result is much better than the hand-calculation expectation.

There are many reasons that could lead to this result.

1. In hand-calculation, the body effect is ignored which means the actual value of  $R_{out}$  is much smaller than the expected one.
2. The channel length modulation of short channel transistor is much different with a long channel one, which means its performance is not as predictable as a normal one.
3. The threshold voltage  $V_{th}$  is enlarged because of the body effect, and it will lead to the decrease of  $g_m$ .

### Complete Circuit

With the designs above, the complete circuit is shown in Figure (11).

To erase the DC effect of the former stage, all stage are isolated with each other by a capacitor with the capacitance of 18nF. However, it will have an effect to the AC circuit since a capacitor will have an impedance as  $Z_C = \frac{1}{j\omega C}$  [4]. The AC circuit diagram is shown in Figure (12).

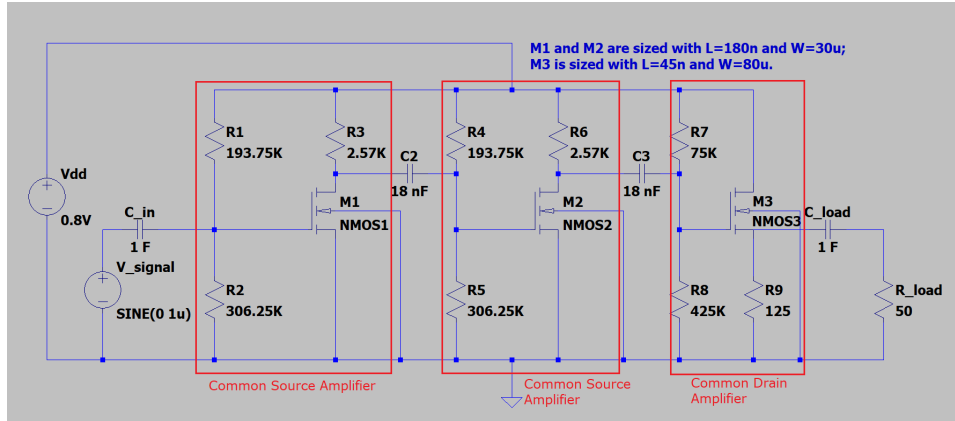


Figure 11: Complete Circuit with Stage Division

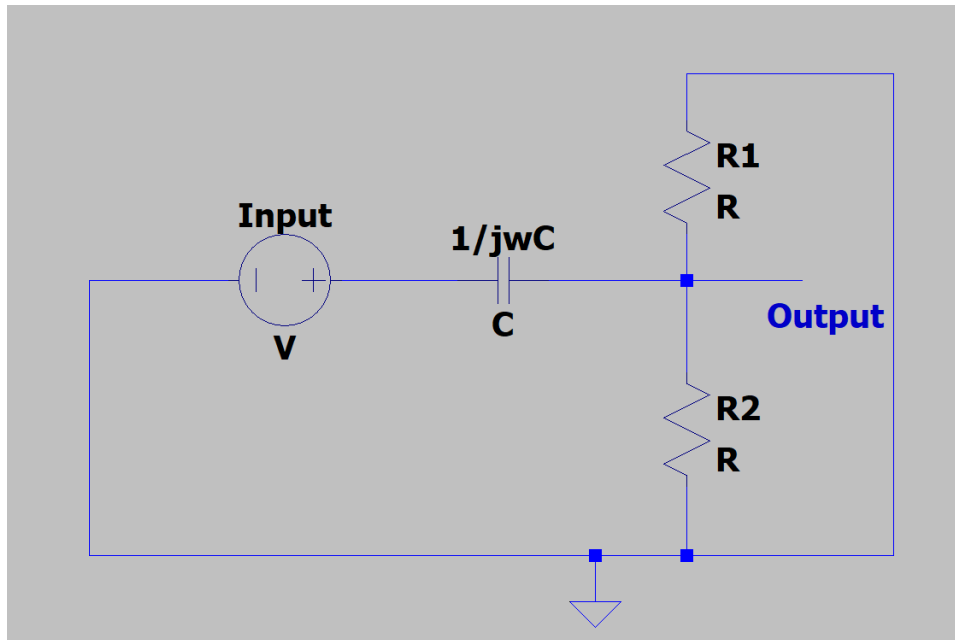


Figure 12: AC Circuit with Capacitor

To erase the AC effect from the capacitor, one way is to increase the value of voltage divider's resistors. It is also for the power consumption consideration since the larger resistance will have less power consumption if the voltage is fixed.

## Conclusion

In conclusion, this design contains two identical common source stages and one common drain stage. For each stage, the parameter setting and some of the results are shown in Table (8).

Table 8: Parameter Setting & Some Results

	$V_{GS}(\text{mV})$	$W(\mu\text{m})$	$L(\text{nm})$	$R_D/R_S(\Omega)$	$V_{DS}(\text{mV})$	$I_d(\text{A})$
CS	488.2	30	180	2.57k	203	$232.2 \times 10^{-6}$
CD	679.6	80	45	125	543.3	$2.085 \times 10^{-3}$

The DC simulation is shown in Figure (13) and the AC gain simulation is shown in Figure (14). The DC gain is about 30.35dB, which fits the requirement. The power consumption in all is about  $824.95 \mu\text{W}$ .

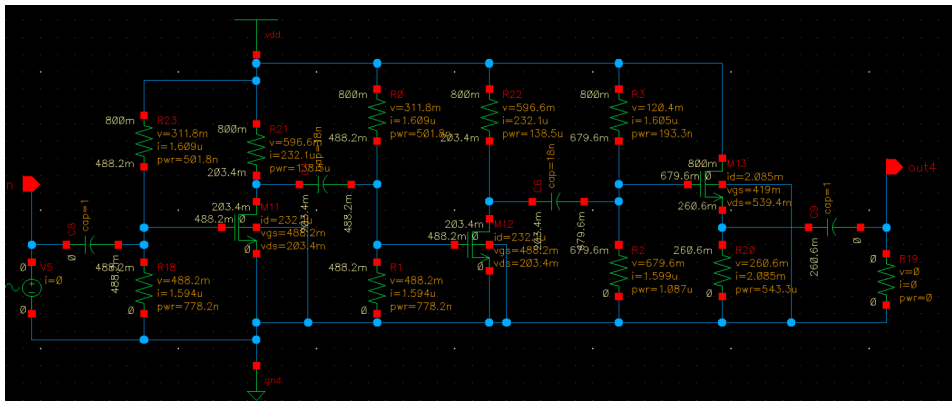


Figure 13: DC Simulation of Complete Circuit

 


Figure 14: AC Simulation of Complete Circuit

## References

1. A. Agarwal and J. Lang. *Foundations of Analog and Digital Electronic Circuits*. The Morgan Kaufmann Series in Computer Architecture and Design. Elsevier Science, 2005.
2. D. Crecraft and D. Gorham. *Electronics, 2nd Edition*. Taylor & Francis, 2003.
3. A.S. Sedra and K.C. Smith. *Microelectronic Circuits*. The Oxford Series in Electrical and Computer Engineering. Oxford University Press, 2015.
4. C. Alexander and M. Sadiku. *Fundamentals of Electric Circuits: Fifth Edition*. Prentice Hall, 2012.